

Project 3: 2-Bit Saturating Counter

E210/B441, Spring 2021

Version 2021.0

Autograder Due: 11:59PM, Friday February 26th

Demo Due: 11:59PM, Friday February 26th

Overview

In this lab you practice designing simple state machines by implementing a 2-bit saturating counter.

Background

Saturating Counters

A 2-bit saturating counter is a logic block that is commonly used in modern computers for predicting the outcome of branch instructions. (Don't worry, you don't need to know about branch prediction for this project).

Such a counter is defined as follows:

- It uses two bits to represent an unsigned number. It is capable of counting from 0-3.
- It is capable of counting up (incrementing) or down (decrementing).
- The counter will “saturate” or stay at its current value if asked to increment or decrement out of its range. For example, in this case that means if the counter is asked to count up past 3 it will stay at 3. If it is asked to count down past 0, it will stay at 0.
- A counter with enable can be told to stop counting.


Our device has three 1-bit inputs: `rst`, `enable` and `up_down` and one 2-bit output `count`. When `enable` is 1, an internal counter is to increment if `up_down` is 1 and decrement if `up_down` is 0. When `enable` is 0, the counter should maintain its current value. When `rst` (reset) is 1 the counter should go to 0 no matter what the other inputs might be. All of the above should happen on each rising edge of the clock.

The output `count` should match the internal count value of the saturating counter.

State Machine Verilog Template

Building state machines in Verilog requires **closely following a special form**, or template, that we have demonstrated below. **Be warned: the tools do not enforce this template, it is up to you to write your code correctly!**

 Here is a simple state machine with one input, `x`, and two outputs, `foo` and `bar`. The inputs are shown in red and the outputs are blue.



Notice that the outputs `bar` and `foo` are set differently. The value of `bar` can be assigned based entirely on the current state (`STATE_ONE`), making it a Moore-type output. The value of `foo` requires both state (`STATE_TWO`) and the input (`x`), making it a Mealy-type output. A second interesting note is that two of the states, `STATE_IDLE` and `STATE_TWO`, have a guard to control their state transitions. If `x` is 0 (shown as `!x`) the state remains unchanged. If `x` is 1 (or just `x`), then the state transitions on the next clock edge. `STATE_ONE` does not have a guard (shown as `-`). This means it always transitions to the next state on the clock edge.

The Verilog implementation of the state machine is provided below.

```
module SimpleStateMachine(
    input      clk, // clock signal
    input      rst, // reset signal
    input logic x,  // input signal
    output logic bar, // Moore-type output
    output logic foo // Mealy-type output
);
```

```

//STATE NAMES
// States can be named whatever you want.
enum { STATE_IDLE, STATE_ONE, STATE_TWO } state, nextState;

//sequential block, uses Flip-Flops
// This always uses Non-Blocking (<=) assignments
always_ff @(posedge clk) begin
    //reset is the only if() case we suggest in always_ff
    if (rst)
        state <= STATE_IDLE; //add a reset case
    else
        state <= nextState; //non-blocking
end

//combinational logic block
//This always uses blocking (=) assignments
//You need a default value for everything assigned
// to avoid inferring a latch
always_comb begin

    //defaults
    // Don't forget these!
    // Otherwise you will end up with a latch
    nextState = state; //DO NOT FORGET DEFAULTS
    bar = 'h0; //DO NOT FORGET DEFAULTS
    foo = 'h0; //DO NOT FORGET DEFAULTS

    case(state)
    STATE_IDLE:
        //only transition to STATE_ONE if x is true
        if (x)
            nextState = STATE_ONE; //blocking
        else //optional, handed by default
            nextState = STATE_IDLE; //blocking
    STATE_ONE:
        nextState = STATE_TWO; //blocking
        bar = 'h1; //dependent on only state, not input
    STATE_TWO: begin
        if (x) begin
            nextState = STATE_IDLE; //blocking
            foo = 'h1; //dependent on state + input
        end else begin //optional
            nextState = STATE_TWO;
            foo = 'h0;
        end
    end
end

```

```
        default:  nextState = STATE_IDLE; //case-default
    endcase
end

endmodule
```

Testbenches for Sequential Logic

When constructing testbenches for sequential logic, you may find the `@(negedge clk)` formulation helpful. This will execute the simulation until the next falling edge of the clock signal. At this point, all the output signals should be stable, allowing you to test them without having to know the exact `#delay` values necessary. With this you can skip forward a considerable time in the simulation. An example testbench for the above state machine is given below.

```
`timescale 1ns / 1ps

module testbench;

    logic      clk, rst, x;
    wire       bar, foo;

    SimpleStateMachine ssm0(
        .clk,
        .rst,
        .x,
        .bar,
        .foo
    );

    task test_logic( input barT, fooT);
    #1 //let input changes settle
    assert( bar == barT) else $fatal("Bad bar");
    assert( foo == fooT) else $fatal("Bad foo");
    endtask

    //inverts the clock signal for 100MHz clock
    always #5 clk = ~clk;

    initial begin
        // set initial values for clk and reset
        // Always start with rst = 1 for at least 1 clock cycle
```

```

clk = 0;
rst = 1;
x = 0;

$monitor ("clk:%b rst:%b x:%b foo:%b bar:%b",
          clk, rst, x, foo, bar);

// wait a few clock cycles
// and then clear reset
for (int i = 0; i < 8; ++i)
    @(negedge clk);

$display(" transition to STATE_ONE");
rst = 0;
x = 1;
test_logic ( 'h0, 'h0); //mealy-type test
@(negedge clk);
test_logic ( 'h1, 'h0); //moore-type test

$display(" transition to STATE_TWO");
x = 0;
test_logic ( 'h1, 'h0); //mealy-type test
@(negedge clk);
test_logic ( 'h0, 'h0); //moore-type test

$display(" stay at STATE_TWO");
x = 0;
test_logic ( 'h0, 'h0); //mealy-type test
@(negedge clk);
test_logic ( 'h0, 'h0); //moore-type test

$display(" transition to STATE_IDLE");
x = 1;
test_logic ( 'h0, 'h1); //mealy-type test
@(negedge clk);
test_logic ( 'h0, 'h0); //moore-type test

$display(" stay at STATE_IDLE");
x = 0;
test_logic ( 'h0, 'h0); //mealy-type test
@(negedge clk);
test_logic ( 'h0, 'h0); //moore-type test

$display("@@@Passed\n");
$finish;

end

```

```
endmodule
```

Assignment Description

For this assignment, you will create and demonstrate a saturating counter.

Saturating Counter

Your first task is to create a Verilog file named `saturating_counter.sv` with a module defined as follows:

```
module saturating_counter(  
    input    clk,  
    input    rst,  
    input    enable,  
    input    up_down, //1 for up, 0 for down  
    output logic [1:0] count  
);
```

This module should implement a saturating counter as described above.

Debouncing

Sometimes digital buttons (like on the Basys3) don't go straight between logic values, but instead "bounce" around while you are trying to change them.

[More Information about Bouncing](#)

Please add this Verilog module to your project to help "debounce" incoming signals.

[debounce.sv](#)

Top-Level

Please use the following `top.sv`. It maps `reset` to `btnC`, `up_down` to `sw[0]`, and `enable` to `btnD`. It also debounces and limits the `enable` signal.

```
`timescale 1ns / 1ps
```

```

module top (
    input CLK100MHZ, //clk
    input btnC, //reset

    input btnD, //enable
    input [15:0] sw,

    output logic [15:0] LED

);

wire clk = CLK100MHZ;
wire rst = btnC;
wire stable;
logic enable;
wire [1:0] count;

// Debounce our incoming signal
debounce db0 (
    .clk(clk),
    .rst(rst),
    .bouncy(btnD),
    .stable(stable)
);

// Then limit enable high to 1 clock cycle
enum {ST_IDLE, ST_WAIT} state, nextState;

always_ff @(posedge clk) begin
    if (rst)
        state <= ST_IDLE;
    else
        state <= nextState;
end

always_comb begin
    nextState = state;
    enable = 'h0;
    case (state)
        ST_IDLE: begin
            if (stable) begin
                enable = 'h1;
                nextState = ST_WAIT;
            end
        end
    end
end

```

```

        ST_WAIT:  if (!stable) nextState = ST_IDLE;
    endcase
end

//finally our saturating counter
saturating_counter sCnt0(
    .clk(clk),
    .rst(rst),
    .enable(enable),
    .up_down(sw[0]),
    .count(count)
);

//decoder for the output
always_comb begin
    LED = 16'h0;
    LED[count] = 1'h1;
end

endmodule

```

Testbench

For this project, you only need to create a testbench for your saturating counter. It should be named `saturating_counter_tb.sv`.

Remember to select “System Verilog” from the “File Type” drop-down menu.

Constraints

We recommend you copy the default constraints file from here:

[Basys3 Constraints](#)

You will also need to reconfigure your file to align with the top-level module declaration. The names should line up properly by default.

Evaluation

NOTE: Due to COVID and working remotely, we will delay the demonstration portion of this project until in-person labs resume.

The evaluation will have two steps, first submission of your source code and testbench to the autograder. Second, you will need to synthesize your design, download it to the FPGA and do a demonstration for the TA.

Autograder (70%)

Log on to <https://autograder.sice.indiana.edu> and submit your code as per Project 1.

You should submit:

- `saturating_counter.sv`
- `saturating_counter_tb.sv`

Demonstration (30%)

~~Program your FPGA with your demultiplexer and demonstrate your working system to the TA. You will not receive full points until the TA has approved your demonstration.~~

For your demonstration, you will need to create a short (~30 second) video and upload it to Canvas.

Please generate the bitstream and program the FPGA as described in Project 0.

After programming your FPGA, you will need to make a video of you using your FPGA board.

For full points, this video **must** include the following sequence (in order):

- Resetting the FPGA using the center button.
- Incrementing the counter from 0 to 3, updating the LEDs.
- Incrementing the counter while already at 3, not updating the LEDs.
- Decrementing the counter from 3 to 0, updating the LEDs.
- Decrementing the counter while already at 0, not updating the LEDs.
- Incrementing the counter from 0 to 2, updating the LEDs,
- Decrementing the counter from 2 to 1, updating the LEDs,
- Incrementing the counter from 1 to 3, updating the LEDs.

Upload your video on Canvas. You can submit the video as a media recording (.mp4, .avi) or a zip file containing the media recording.